

Relatório

Tópico: Aula 4 & 5 - Contadores

Grupo: Frederico Scheffel Oliveira 15452718

Leonardo Massuhiro Sato 15469108

Pedro Henrique Perez Dias 15484075

Github: https://github.com/johncleyton/SistemasDigitais/tree/main/Aula_4-5

Parte 1

1.1)

Código VHDL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity T_FF is
    Port (
        clk      : in  std_logic;
        clear    : in  std_logic; -- Synchronous clear
        T        : in  std_logic; -- Enable to toggle
        Q        : out std_logic;
        Q_n      : out std_logic
    );
end T_FF;
```

```
architecture Behavioral of T_FF is
    signal Q_int : std_logic := '0';
begin
    process(clk, clear)
    begin
        if clear = '0' then
            Q_int <= '0';
        elsif rising_edge(clk) then
            if T = '1' then
                Q_int <= not Q_int;
            end if;
        end if;
    end process;
```

```
    Q      <= Q_int;
    Q_n    <= not Q_int;
end Behavioral;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Counter8bit is
    Port (
        clk      : in  std_logic;
        clear    : in  std_logic;
        enable   : in  std_logic;
        count    : out std_logic
    );
end Counter8bit;
```

```
architecture Behavioral of Counter8bit is
    signal Q : std_logic_vector(7 downto 0);
```

```

signal Q_n : std_logic_vector(7 downto 0);
signal enable_internal : std_logic_vector(7 downto 0);

begin

    -- Generate enable signals for each flip-flop
    enable_internal(0) <= enable; -- First flip-flop
    enable_internal(1) <= Q(0) and enable_internal(0);
    enable_internal(2) <= Q(1) and enable_internal(1);
    enable_internal(3) <= Q(2) and enable_internal(2);
    enable_internal(4) <= Q(3) and enable_internal(3);
    enable_internal(5) <= Q(4) and enable_internal(4);
    enable_internal(6) <= Q(5) and enable_internal(5);
    enable_internal(7) <= Q(6) and enable_internal(6);


    gen_ff: for i in 0 to 7 generate
    T_FF_inst : entity work.T_FF
    Port map (
        clk      => clk,
        clear    => clear,
        T        => enable_internal(i),
        Q        => Q(i),
        Q_n      => Q_n(i)
    );
    end generate;

    count <= Q(7);

end Behavioral;


```

RTL Viewer - Contador de 8 bits

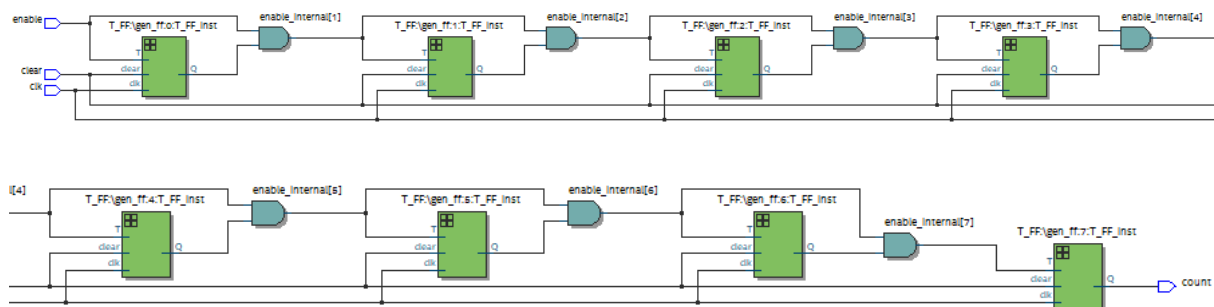

1.2)

Simulação do contador de 8 bits

 

1.3)

Código VHDL do display de 7 segmentos

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

Library work;

ENTITY display_7seg IS
    PORT
    (
        input1 : IN STD_LOGIC;
        input2 : IN STD_LOGIC;
        input3 : IN STD_LOGIC;
        input4 : IN STD_LOGIC;
        output0 : OUT STD_LOGIC;
        output1 : OUT STD_LOGIC;
        output2 : OUT STD_LOGIC;
        output3 : OUT STD_LOGIC;
        output4 : OUT STD_LOGIC;
        output5 : OUT STD_LOGIC;
        output6 : OUT STD_LOGIC
    );
END display_7seg;

ARCHITECTURE bdf_type OF display_7seg IS

    SIGNAL FIO1 : STD_LOGIC;
    SIGNAL FIO2 : STD_LOGIC;
    SIGNAL FIO3 : STD_LOGIC;
    SIGNAL FIO4 : STD_LOGIC;
    SIGNAL fio_final0 : STD_LOGIC;
    SIGNAL fio_final1 : STD_LOGIC;
    SIGNAL fio_final2 : STD_LOGIC;
    SIGNAL fio_final3 : STD_LOGIC;
    SIGNAL fio_final4 : STD_LOGIC;
    SIGNAL fio_final5 : STD_LOGIC;
    SIGNAL fio_final6 : STD_LOGIC;
    SIGNAL fio_numero0 : STD_LOGIC;
    SIGNAL fio_numero1 : STD_LOGIC;
    SIGNAL fio_numero2 : STD_LOGIC;
    SIGNAL fio_numero3 : STD_LOGIC;
    SIGNAL fio_numero4 : STD_LOGIC;
    SIGNAL fio_numero5 : STD_LOGIC;
    SIGNAL fio_numero6 : STD_LOGIC;
    SIGNAL fio_numero7 : STD_LOGIC;
    SIGNAL fio_numero8 : STD_LOGIC;
    SIGNAL fio_numero9 : STD_LOGIC;
    SIGNAL fio_numeroA : STD_LOGIC;
    SIGNAL fio_numeroB : STD_LOGIC;
    SIGNAL fio_numeroC : STD_LOGIC;
    SIGNAL fio_numeroD : STD_LOGIC;
    SIGNAL fio_numeroE : STD_LOGIC;
    SIGNAL fio_numeroF : STD_LOGIC;
    SIGNAL NOT1 : STD_LOGIC;
    SIGNAL NOT2 : STD_LOGIC;
    SIGNAL NOT3 : STD_LOGIC;
    SIGNAL NOT4 : STD_LOGIC;
    SIGNAL SYNTHESIZED_WIRE_0 : STD_LOGIC;
```

```
SIGNAL SYNTHESIZED_WIRE_1 : STD_LOGIC;
```

```
BEGIN
```

```
NOT1 <= NOT(FIO1);  
NOT2 <= NOT(FIO2);  
NOT3 <= NOT(FIO3);  
NOT4 <= NOT(FIO4);
```

```
fio_final0 <= fio_numero1 OR fio_numeroB OR fio_numeroD OR fio_numero4;  
fio_final1 <= fio_numero5 OR fio_numeroB OR fio_numero6 OR fio_numeroC OR fio_numeroE OR fio_numeroF;  
fio_final2 <= fio_numero2 OR fio_numeroE OR fio_numeroF OR fio_numeroC;  
SYNTHESIZED_WIRE_0 <= fio_numero4 OR fio_numero1;  
fio_final3 <= SYNTHESIZED_WIRE_0 OR fio_numeroA OR fio_numeroF OR fio_numero7;  
fio_final4 <= fio_numero1 OR fio_numero4 OR fio_numero3 OR fio_numero5 OR fio_numero7 OR fio_numero9;  
SYNTHESIZED_WIRE_1 <= fio_numero2 OR fio_numero1;  
fio_final5 <= SYNTHESIZED_WIRE_1 OR fio_numero7 OR fio_numeroD OR fio_numero3;  
fio_final6 <= fio_numero0 OR fio_numero7 OR fio_numeroC OR fio_numero1;
```

```
fio_numero0 <= NOT1 AND NOT2 AND NOT3 AND NOT4;  
fio_numero1 <= FIO1 AND NOT2 AND NOT3 AND NOT4;  
fio_numero2 <= NOT1 AND FIO2 AND NOT3 AND NOT4;  
fio_numero3 <= FIO1 AND FIO2 AND NOT3 AND NOT4;  
fio_numero4 <= NOT1 AND NOT2 AND FIO3 AND NOT4;  
fio_numero5 <= FIO1 AND NOT2 AND FIO3 AND NOT4;  
fio_numero6 <= NOT1 AND FIO2 AND FIO3 AND NOT4;  
fio_numero7 <= FIO1 AND FIO2 AND FIO3 AND NOT4;  
fio_numero9 <= FIO1 AND NOT2 AND NOT3 AND FIO4;  
fio_numeroA <= NOT1 AND FIO2 AND NOT3 AND FIO4;  
fio_numeroB <= FIO1 AND FIO2 AND NOT3 AND FIO4;  
fio_numeroC <= NOT1 AND NOT2 AND FIO3 AND FIO4;  
fio_numeroD <= FIO1 AND NOT2 AND FIO3 AND FIO4;  
fio_numeroE <= NOT1 AND FIO2 AND FIO3 AND FIO4;  
fio_numeroF <= FIO1 AND FIO2 AND FIO3 AND FIO4;
```

```
output0 <= fio_final0;  
FIO1 <= input1;  
FIO2 <= input2;  
FIO3 <= input3;  
FIO4 <= input4;  
output1 <= fio_final1;  
output2 <= fio_final2;  
output3 <= fio_final3;  
output4 <= fio_final4;  
output5 <= fio_final5;  
output6 <= fio_final6;
```

```
END bdf_type;
```

Código completo da parte 1 - Counter8bit + display_7seg:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity T_FF is
    Port (
        clk      : in  std_logic;
        clear    : in  std_logic; -- Synchronous clear
        T        : in  std_logic; -- Enable to toggle
        Q        : out std_logic;
        Q_n      : out std_logic
    );
end T_FF;

```

```

architecture Behavioral of T_FF is
    signal Q_int : std_logic := '0';
begin
    process(clk, clear)
    begin
        if clear = '0' then
            Q_int <= '0';
        elsif rising_edge(clk) then
            if T = '1' then
                Q_int <= not Q_int;
            end if;
        end if;
    end process;

    Q      <= Q_int;
    Q_n    <= not Q_int;
end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity Counter8bit is
    Port (
        clk      : in  std_logic;
        clear    : in  std_logic;
        enable    : in  std_logic;
        count    : out std_logic_vector(7 downto 0);
        hex00    : out std_logic;
        hex01    : out std_logic;
        hex02    : out std_logic;
        hex03    : out std_logic;
        hex04    : out std_logic;
        hex05    : out std_logic;
        hex06    : out std_logic;
        hex10    : out std_logic;
        hex11    : out std_logic;
        hex12    : out std_logic;
        hex13    : out std_logic;
        hex14    : out std_logic;
        hex15    : out std_logic;
        hex16    : out std_logic
    );
end Counter8bit;

```

```

architecture Behavioral of Counter8bit is

```

```

signal Q : std_logic_vector(7 downto 0);
signal Q_n : std_logic_vector(7 downto 0);
signal enable_internal : std_logic_vector(7 downto 0);

```

component display_7seg is

Port

```

(
    input1 : IN STD_LOGIC;
    input2 : IN STD_LOGIC;
    input3 : IN STD_LOGIC;
    input4 : IN STD_LOGIC;
    output0 : OUT STD_LOGIC;
    output1 : OUT STD_LOGIC;
    output2 : OUT STD_LOGIC;
    output3 : OUT STD_LOGIC;
    output4 : OUT STD_LOGIC;
    output5 : OUT STD_LOGIC;
    output6 : OUT STD_LOGIC
);
end component;

```

begin

```

-- Generate enable signals for each flip-flop
enable_internal(0) <= enable; -- First flip-flop
enable_internal(1) <= Q(0) and enable_internal(0);
enable_internal(2) <= Q(1) and enable_internal(1);
enable_internal(3) <= Q(2) and enable_internal(2);
enable_internal(4) <= Q(3) and enable_internal(3);
enable_internal(5) <= Q(4) and enable_internal(4);
enable_internal(6) <= Q(5) and enable_internal(5);
enable_internal(7) <= Q(6) and enable_internal(6);

```

```

-- Instantiate 8 T flip-flops
gen_ff: for i in 0 to 7 generate
    T_FF_inst : entity work.T_FF
    Port map (
        clk      => clk,
        clear    => clear,
        T        => enable_internal(i),
        Q        => Q(i),
        Q_n      => Q_n(i)
    );
end generate;

```

display_7_min : entity work.display_7seg

```

    Port map (
        input1 => Q(0),
        input2 => Q(1),
        input3 => Q(2),
        input4 => Q(3),
        output0 => hex00,
        output1 => hex01,
        output2 => hex02,
        output3 => hex03,
        output4 => hex04,
        output5 => hex05,
        output6 => hex06
    );

```

```

display_7_max : entity work.display_7seg
  Port map (
    input1 => Q(4),
    input2 => Q(5),
    input3 => Q(6),
    input4 => Q(7),
    output0 => hex10,
    output1 => hex11,
    output2 => hex12,
    output3 => hex13,
    output4 => hex14,
    output5 => hex15,
    output6 => hex16
  );

  count <= Q;

end Behavioral;

```

1.5)

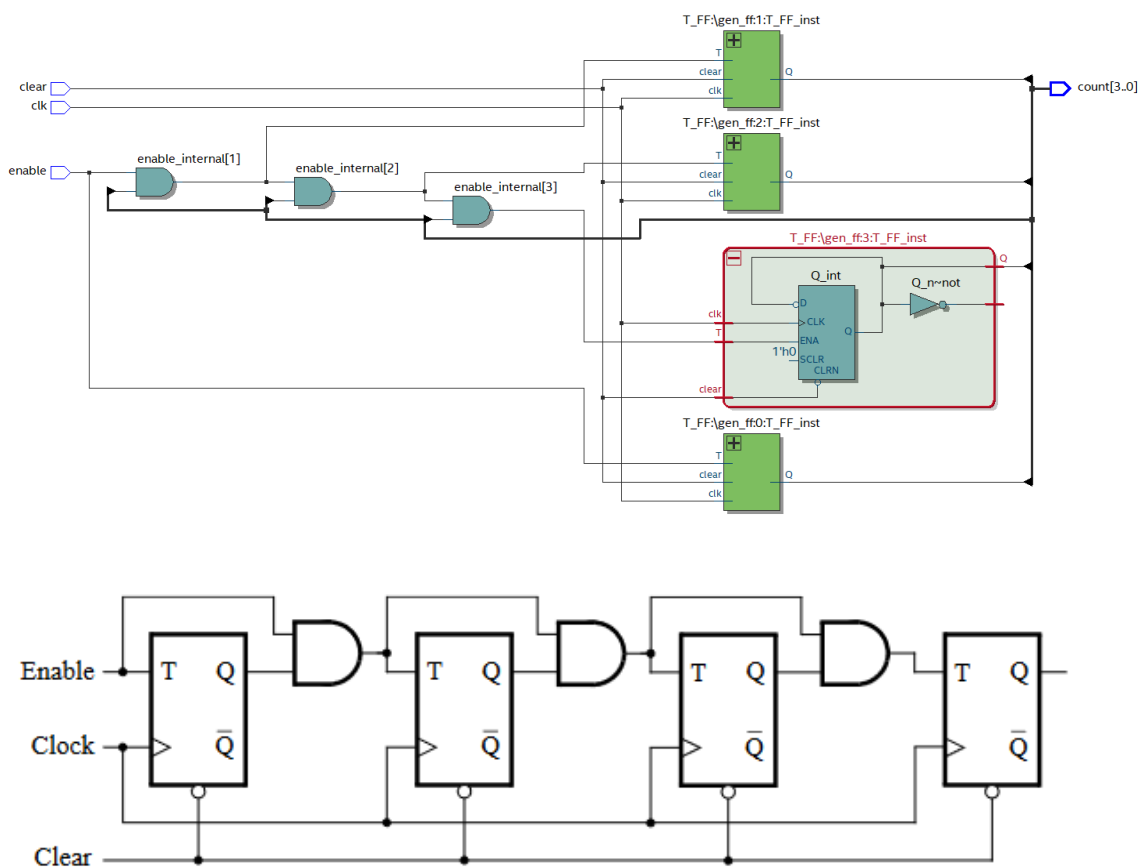


Figure 1: A 4-bit counter.

Ao analisarmos o circuito de 4 bits pelo RTL viewer, é perceptível que não houve uma grande mudança no próprio sistema de portas lógicas, com exceção do nosso output ser mais compacto, utilizando um vetor de outputs, e também pelo modo de como os fios foram

conectados, que parece mais caótico no RTL viewer, apesar de manter a mesma função do sistema.

Parte 2

Código VHDL - 4 Displays de 7 segmentos, usando contador de 16 bits

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter16bit is
    Port (
        clk : in std_logic;
        clear : in std_logic;
        enable : in std_logic;
        count : out std_logic_vector(15 downto 0);
        hex00 : out std_logic;
        hex01 : out std_logic;
        hex02 : out std_logic;
        hex03 : out std_logic;
        hex04 : out std_logic;
        hex05 : out std_logic;
        hex06 : out std_logic;
        hex10 : out std_logic;
        hex11 : out std_logic;
        hex12 : out std_logic;
        hex13 : out std_logic;
        hex14 : out std_logic;
        hex15 : out std_logic;
        hex16 : out std_logic;
        hex20 : out std_logic;
        hex21 : out std_logic;
        hex22 : out std_logic;
        hex23 : out std_logic;
        hex24 : out std_logic;
        hex25 : out std_logic;
        hex26 : out std_logic;
        hex30 : out std_logic;
        hex31 : out std_logic;
        hex32 : out std_logic;
        hex33 : out std_logic;
        hex34 : out std_logic;
        hex35 : out std_logic;
        hex36 : out std_logic
    );
end Counter16bit;

architecture Behavioral of Counter16bit is
    signal Q : std_logic_vector(15 downto 0);

    component display_7seg is
        Port
        (
            input1 : IN STD_LOGIC;
            input2 : IN STD_LOGIC;
            input3 : IN STD_LOGIC;
```



```

        input4 : IN STD_LOGIC;
        output0 : OUT STD_LOGIC;
        output1 : OUT STD_LOGIC;
        output2 : OUT STD_LOGIC;
        output3 : OUT STD_LOGIC;
        output4 : OUT STD_LOGIC;
        output5 : OUT STD_LOGIC;
        output6 : OUT STD_LOGIC
    );
end component;

begin

    process(clk)
    begin
        if clear = '0' then
            Q <= "0000000000000000";
        elsif rising_edge(clk) then
            if enable = '1' then
                Q <= std_logic_vector(unsigned(Q) + 1);
            end if;
        end if;
    end process;

    display_7_1 : entity work.display_7seg
        Port map (
            input1 => Q(0),
            input2 => Q(1),
            input3 => Q(2),
            input4 => Q(3),
            output0 => hex00,
            output1 => hex01,
            output2 => hex02,
            output3 => hex03,
            output4 => hex04,
            output5 => hex05,
            output6 => hex06
        );

    display_7_2 : entity work.display_7seg
        Port map (
            input1 => Q(4),
            input2 => Q(5),
            input3 => Q(6),
            input4 => Q(7),
            output0 => hex10,
            output1 => hex11,
            output2 => hex12,
            output3 => hex13,
            output4 => hex14,
            output5 => hex15,
            output6 => hex16
        );

    display_7_3 : entity work.display_7seg
        Port map (
            input1 => Q(8),
            input2 => Q(9),
            input3 => Q(10),
            input4 => Q(11),

```

```

        output0 => hex20,
        output1 => hex21,
        output2 => hex22,
        output3 => hex23,
        output4 => hex24,
        output5 => hex25,
        output6 => hex26

    );
display_7_4 : entity work.display_7seg
    Port map (
        input1 => Q(12),
        input2 => Q(13),
        input3 => Q(14),
        input4 => Q(15),
        output0 => hex30,
        output1 => hex31,
        output2 => hex32,
        output3 => hex33,
        output4 => hex34,
        output5 => hex35,
        output6 => hex36


    );

    count <= Q;

```

end Behavioral;

RTL Viewer - Contador de 16 bits

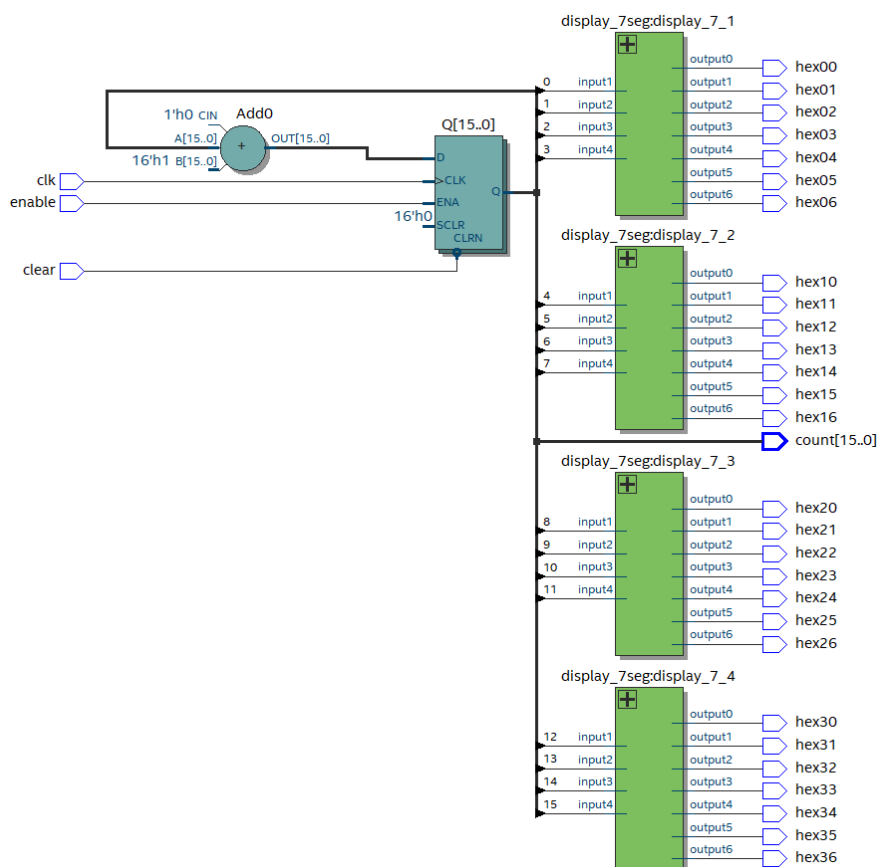

Se compararmos as estruturas desse componente com a do anteriormente desenvolvido, pode-se observar que cada bit possui seu próprio contador. Além disso, percebe-se que o

circuito com registradores é mais simples do que o que utiliza flip-flops T, possuindo menos estruturas e portas lógicas para realizar o mesmo tipo de problema.

Parte 3

Por estar na frequência de 50MHz, foi necessário comparar os valores do “clock” da placa com "10111110101111000010000000" (50 milhões em binário), para atualizar o contador que seria exibido no display

Código VHDL - Contador de 0 a 9, usando o clock da FPGA

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter10 is
    Port (
        clk : in std_logic;
        clear : in std_logic;
        enable : in std_logic;
        count : out std_logic_vector(3 downto 0);
        hex00 : out std_logic;
        hex01 : out std_logic;
        hex02 : out std_logic;
        hex03 : out std_logic;
        hex04 : out std_logic;
        hex05 : out std_logic;
        hex06 : out std_logic
    );
end Counter10;

architecture Behavioral of Counter10 is
    -- Representa o clock da FPGA
    signal fpgaCounter : std_logic_vector(25 downto 0);
    -- Representa os números do display
    signal displayCounter : std_logic_vector(3 downto 0);

    component display_7seg is
        Port
        (
            input1 : IN STD_LOGIC;
            input2 : IN STD_LOGIC;
            input3 : IN STD_LOGIC;
            input4 : IN STD_LOGIC;
            output0 : OUT STD_LOGIC;
            output1 : OUT STD_LOGIC;
            output2 : OUT STD_LOGIC;
            output3 : OUT STD_LOGIC;
            output4 : OUT STD_LOGIC;
            output5 : OUT STD_LOGIC;
            output6 : OUT STD_LOGIC
        );
    end component;

begin
```

```

process(clk)
begin
if (rising_edge(clk)) then
if (Clear = '0') then
fpgaCounter <= "00000000000000000000000000000000";
displayCounter <= "0000";

elsif (enable = '1') then
fpgaCounter <= std_logic_vector(unsigned(fpgaCounter) + 1);
-- 50MHz -> 50 milhões de 'ticks' da placa, ou seja, 1 segundo alterado no display
if (fpgaCounter = "10111110101111000010000000") then
-- printar no máximo até 9
if (displayCounter = "1001") then
displayCounter <= "0000";

else
displayCounter <= displayCounter + 1;
end if;
fpgaCounter <= "00000000000000000000000000000000";
end if;

else
fpgaCounter <= fpgaCounter;
end if;
end if;
end process;

```

```

display_7_1 : entity work.display_7seg
Port map (
input1 => displayCounter(0),
input2 => displayCounter(1),
input3 => displayCounter(2),
input4 => displayCounter(3),
output0 => hex00,
output1 => hex01,
output2 => hex02,
output3 => hex03,
output4 => hex04,
output5 => hex05,
output6 => hex06
);

```

```

count <= displayCounter;

```

```

end Behavioral;

```

Parte 4

Nesse exercício foi utilizado o mecanismo de clock desenvolvido na parte 3, utilizando o clock de 50MHz da placa.

Código VHDL - Rotacionar palavra entre 3 displays

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity RotateOnFourDisplays is

```

```

Port (
    clk : in std_logic;
    clear : in std_logic;
    enable : in std_logic;
    count : out std_logic_vector(1 downto 0);
        hex00 : out std_logic;
        hex01 : out std_logic;
        hex02 : out std_logic;
        hex03 : out std_logic;
        hex04 : out std_logic;
        hex05 : out std_logic;
        hex06 : out std_logic;
        hex10 : out std_logic;
        hex11 : out std_logic;
        hex12 : out std_logic;
        hex13 : out std_logic;
        hex14 : out std_logic;
        hex15 : out std_logic;
        hex16 : out std_logic;
        hex20 : out std_logic;
        hex21 : out std_logic;
        hex22 : out std_logic;
        hex23 : out std_logic;
        hex24 : out std_logic;
        hex25 : out std_logic;
        hex26 : out std_logic
);
end RotateOnFourDisplays;

architecture Behavioral of RotateOnFourDisplays is
    -- Representa o clock da FPGA
    signal fpgaCounter : std_logic_vector(25 downto 0);
    -- Representa os números do display
    signal displayCounter : std_logic_vector(1 downto 0);

    signal display1 : std_logic_vector(3 downto 0);
    signal display2 : std_logic_vector(3 downto 0);
    signal display3 : std_logic_vector(3 downto 0);

    component display_7seg is
        Port
        (
            input1 : IN STD_LOGIC;
            input2 : IN STD_LOGIC;
            input3 : IN STD_LOGIC;
            input4 : IN STD_LOGIC;
            output0 : OUT STD_LOGIC;
            output1 : OUT STD_LOGIC;
            output2 : OUT STD_LOGIC;
            output3 : OUT STD_LOGIC;
            output4 : OUT STD_LOGIC;
            output5 : OUT STD_LOGIC;
            output6 : OUT STD_LOGIC
        );
    end component;

begin

```

```

        process(clk)
        begin
            if (rising_edge(clk)) then
                if (Clear = '0') then
                    fpgaCounter <= "000000000000000000000000";
                    displayCounter <= "00";

                elsif (enable = '1') then
                    fpgaCounter <= std_logic_vector(unsigned(fpgaCounter) + 1);
                    -- 50MHz -> 50 milhões de 'ticks' da placa, ou seja, 1 segundo alterado no display
                    if (fpgaCounter = "10111101011110000100000000") then
                        if (displayCounter = "11") then
                            displayCounter <= "00";
                        end if;
                        case displayCounter is
                            when "00" => display1 <= "0000"; display2 <= "1110"; display3
<= "1101";
                            when "01" => display1 <= "1101"; display2 <= "0000"; display3
<= "1110";
                            when "10" => display1 <= "1110"; display2 <= "1101"; display3
<= "0000";
                            when others => display1 <= "0000"; display2 <= "1110";

                        end case;
                        displayCounter <= displayCounter + 1;
                        fpgaCounter <= "000000000000000000000000";
                    end if;

                else
                    fpgaCounter <= fpgaCounter;
                end if;
            end process;

            display_7_1 : entity work.display_7seg
                Port map (
                    input1 => display1(0),
                    input2 => display1(1),
                    input3 => display1(2),
                    input4 => display1(3),
                    output0 => hex00,
                    output1 => hex01,
                    output2 => hex02,
                    output3 => hex03,
                    output4 => hex04,
                    output5 => hex05,
                    output6 => hex06
                );

            display_7_2 : entity work.display_7seg
                Port map (
                    input1 => display2(0),
                    input2 => display2(1),
                    input3 => display2(2),
                    input4 => display2(3),
                    output0 => hex10,
                    output1 => hex11,
                    output2 => hex12,
                    output3 => hex13,
                    output4 => hex14,

```

```

        output5 => hex15,
        output6 => hex16
    );

display_7_3 : entity work.display_7seg
    Port map (
        input1 => display3(0),
        input2 => display3(1),
        input3 => display3(2),
        input4 => display3(3),
        output0 => hex20,
        output1 => hex21,
        output2 => hex22,
        output3 => hex23,
        output4 => hex24,
        output5 => hex25,
        output6 => hex26
    );

    count <= displayCounter;

end Behavioral;

```

Parte 5

Nesse exercício foi utilizado o mecanismo de clock desenvolvido na parte 3, utilizando o clock de 50MHz da placa.

Código VHDL - Rotacionar palavra entre 6 displays (sem mostrar nada nos outros)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity RotateOnSixDisplays is
    Port (
        clk : in std_logic;
        clear : in std_logic;
        enable : in std_logic;
        count : out std_logic_vector(2 downto 0);
        hex00 : out std_logic;
        hex01 : out std_logic;
        hex02 : out std_logic;
        hex03 : out std_logic;
        hex04 : out std_logic;
        hex05 : out std_logic;
        hex06 : out std_logic;
        hex10 : out std_logic;
        hex11 : out std_logic;
        hex12 : out std_logic;
        hex13 : out std_logic;
        hex14 : out std_logic;
        hex15 : out std_logic;
        hex16 : out std_logic;
        hex20 : out std_logic;
        hex21 : out std_logic;
        hex22 : out std_logic;
    );
end RotateOnSixDisplays;

```

```

        hex23 : out std_logic;
        hex24 : out std_logic;
        hex25 : out std_logic;
        hex26 : out std_logic;
        hex30 : out std_logic;
        hex31 : out std_logic;
        hex32 : out std_logic;
        hex33 : out std_logic;
        hex34 : out std_logic;
        hex35 : out std_logic;
        hex36 : out std_logic;
        hex40 : out std_logic;
        hex41 : out std_logic;
        hex42 : out std_logic;
        hex43 : out std_logic;
        hex44 : out std_logic;
        hex45 : out std_logic;
        hex46 : out std_logic;
        hex50 : out std_logic;
        hex51 : out std_logic;
        hex52 : out std_logic;
        hex53 : out std_logic;
        hex54 : out std_logic;
        hex55 : out std_logic;
        hex56 : out std_logic
    );
end RotateOnSixDisplays;

architecture Behavioral of RotateOnSixDisplays is
    -- Representa o clock da FPGA
    signal fpgaCounter    : std_logic_vector(25 downto 0);
    -- Representa os números do display
    signal displayCounter : std_logic_vector(2 downto 0);

    signal display1      : std_logic_vector(3 downto 0);
    signal display2      : std_logic_vector(3 downto 0);
    signal display3      : std_logic_vector(3 downto 0);
    signal display4      : std_logic_vector(3 downto 0);
    signal display5      : std_logic_vector(3 downto 0);
    signal display6      : std_logic_vector(3 downto 0);

    component display_7seg is
        Port
        (
            input1 : IN STD_LOGIC;
            input2 : IN STD_LOGIC;
            input3 : IN STD_LOGIC;
            input4 : IN STD_LOGIC;
            output0 : OUT STD_LOGIC;
            output1 : OUT STD_LOGIC;
            output2 : OUT STD_LOGIC;
            output3 : OUT STD_LOGIC;
            output4 : OUT STD_LOGIC;
            output5 : OUT STD_LOGIC;
            output6 : OUT STD_LOGIC
        );
    end component;

```



```

begin
    process(clk)
        begin
            if (rising_edge(clk)) then
                if (Clear = '0') then
                    fpgaCounter <= "000000000000000000000000";
                    displayCounter <= "000";

                elsif (enable = '1') then
                    fpgaCounter <= std_logic_vector(unsigned(fpgaCounter) + 1);
                    -- 50MHz -> 50 milhões de 'ticks' da placa, ou seja, 1 segundo alterado no display
                    if (fpgaCounter = "101111010111000010000000") then
                        if (displayCounter = "111") then
                            displayCounter <= "000";
                        end if;
                        case displayCounter is
                            when "000" => display1 <= "0000"; display2 <= "1110";
                        display3 <= "1101"; display4 <= "1111"; display5 <= "1111"; display6 <= "1111";
                            when "001" => display1 <= "1111"; display2 <= "0000";
                        display3 <= "1110"; display4 <= "1101"; display5 <= "1111"; display6 <= "1111";
                            when "010" => display1 <= "1111"; display2 <= "1111";
                        display3 <= "0000"; display4 <= "1110"; display5 <= "1101"; display6 <= "1111";
                            when "011" => display1 <= "1111"; display2 <= "1111";
                        display3 <= "1111"; display4 <= "0000"; display5 <= "1110"; display6 <= "1101";
                            when "100" => display1 <= "1101"; display2 <= "1111";
                        display3 <= "1111"; display4 <= "1111"; display5 <= "0000"; display6 <= "1110";
                            when "101" => display1 <= "1110"; display2 <= "1101";
                        display3 <= "1111"; display4 <= "1111"; display5 <= "1111"; display6 <= "0000";
                            when others => display1 <= "0000"; display2 <= "1110";
                        display3 <= "1101"; display4 <= "1111"; display5 <= "1111"; display6 <= "1111";
                        end case;

                        displayCounter <= displayCounter + 1;
                        fpgaCounter <= "000000000000000000000000";
                    end if;

                else
                    fpgaCounter <= fpgaCounter;
                end if;
            end process;

```

```

display_7_1 : entity work.display_7seg
    Port map (
        input1 => display1(0),
        input2 => display1(1),
        input3 => display1(2),
        input4 => display1(3),
        output0 => hex00,
        output1 => hex01,
        output2 => hex02,
        output3 => hex03,
        output4 => hex04,
        output5 => hex05,
        output6 => hex06
    );

```

```

display_7_2 : entity work.display_7seg
    Port map (

```

```

        input1 => display2(0),
        input2 => display2(1),
        input3 => display2(2),
        input4 => display2(3),
        output0 => hex10,
        output1 => hex11,
        output2 => hex12,
        output3 => hex13,
        output4 => hex14,
        output5 => hex15,
        output6 => hex16
    );

display_7_3 : entity work.display_7seg
    Port map (
        input1 => display3(0),
        input2 => display3(1),
        input3 => display3(2),
        input4 => display3(3),
        output0 => hex20,
        output1 => hex21,
        output2 => hex22,
        output3 => hex23,
        output4 => hex24,
        output5 => hex25,
        output6 => hex26
    );

display_7_4 : entity work.display_7seg
    Port map (
        input1 => display4(0),
        input2 => display4(1),
        input3 => display4(2),
        input4 => display4(3),
        output0 => hex30,
        output1 => hex31,
        output2 => hex32,
        output3 => hex33,
        output4 => hex34,
        output5 => hex35,
        output6 => hex36
    );

display_7_5 : entity work.display_7seg
    Port map (
        input1 => display5(0),
        input2 => display5(1),
        input3 => display5(2),
        input4 => display5(3),
        output0 => hex40,
        output1 => hex41,
        output2 => hex42,
        output3 => hex43,
        output4 => hex44,
        output5 => hex45,
        output6 => hex46
    );

```

```

display_7_6 : entity work.display_7seg
    Port map (
        input1 => display6(0),
        input2 => display6(1),
        input3 => display6(2),
        input4 => display6(3),
        output0 => hex50,
        output1 => hex51,
        output2 => hex52,
        output3 => hex53,
        output4 => hex54,
        output5 => hex55,
        output6 => hex56
    );

```

```

count <= displayCounter;

```

```

end Behavioral;

```

Para esse exercício, foi necessário realizar uma adaptação no display usado anteriormente: adicionando uma verificação para apagar o display quando fosse enviado “1111”, pois no caso não era necessário escrever no display a letra ‘F’.

Foi adicionado esse processo no VHDL do display:

```

PROCESS(input1, input2, input3, input4)
BEGIN
    fio_final0 <= fio_numero1 OR fio_numeroB OR fio_numeroD OR fio_numero4;
    fio_final1 <= fio_numero5 OR fio_numeroB OR fio_numero6 OR fio_numeroC OR fio_numeroE OR
fio_numeroF;
    fio_final2 <= fio_numero2 OR fio_numeroE OR fio_numeroF OR fio_numeroC;
    SYNTHESIZED_WIRE_0 <= fio_numero4 OR fio_numero1;
    fio_final3 <= SYNTHESIZED_WIRE_0 OR fio_numeroA OR fio_numeroF OR fio_numero7;
    fio_final4 <= fio_numero1 OR fio_numero4 OR fio_numero3 OR fio_numero5 OR fio_numero7 OR
fio_numero9;
    SYNTHESIZED_WIRE_1 <= fio_numero2 OR fio_numero1;
    fio_final5 <= SYNTHESIZED_WIRE_1 OR fio_numero7 OR fio_numeroD OR fio_numero3;
    fio_final6 <= fio_numero0 OR fio_numero7 OR fio_numeroC OR fio_numero1;

    if(fio_numeroF = '1') then
        fio_final0 <= '1';
        fio_final1 <= '1';
        fio_final2 <= '1';
        fio_final3 <= '1';
        fio_final4 <= '1';
        fio_final5 <= '1';
        fio_final6 <= '1';
    end if;
end process;

```