


Relatório

Tópico: Aula 2 & 3 - Atividade com Latch e FF
Grupo: Frederico Scheffel Oliveira 15452718
Pedro Henrique Perez Dias 15484075


Parte 1

Attribute keep possibilita verificar valores intermediários de saída das portas lógicas


RTL Viewer:

 

Technology Map Viewer:

 

Simulação no ModelSim

 

Código VHDL:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY part1 IS
PORT ( Clk, R, S : IN STD_LOGIC;
      Q : OUT STD_LOGIC);
END part1;

ARCHITECTURE Structural OF part1 IS
SIGNAL R_g, S_g, Qa, Qb : STD_LOGIC ;
ATTRIBUTE KEEP : BOOLEAN;
ATTRIBUTE KEEP OF R_g, S_g, Qa, Qb : SIGNAL IS TRUE;
```


```

BEGIN
R_g <= R AND Clk;
S_g <= S AND Clk;
Qa <= NOT (R_g OR Qb);
Qb <= NOT (S_g OR Qa);
Q <= Qa;
END Structural;


```

Parte 2

Technology Map Viewer:

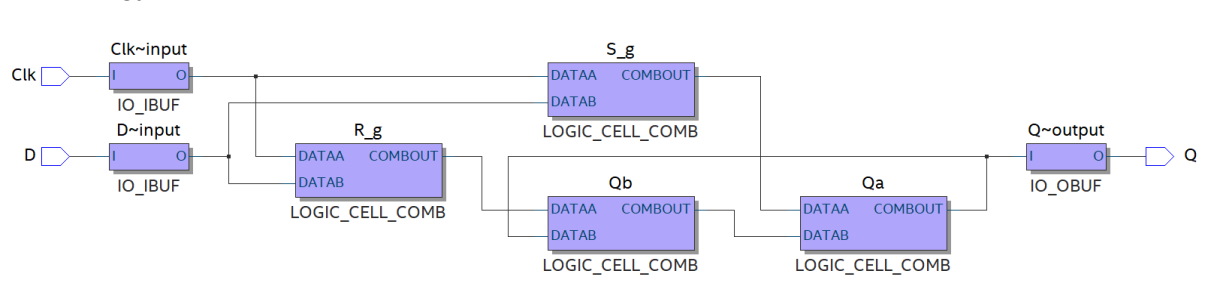

Simulação no ModelSim

 

Código VHDL:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY part2 IS
PORT ( Clk, D : IN STD_LOGIC;
      Q : OUT STD_LOGIC);
END part2;

ARCHITECTURE Structural OF part2 IS
SIGNAL R_g, S_g, Qa, Qb, S, R : STD_LOGIC ;
ATTRIBUTE KEEP : BOOLEAN;
ATTRIBUTE KEEP OF R_g, S_g, Qa, Qb : SIGNAL IS TRUE;
BEGIN
S <= D;
R <= NOT (D);
R_g <= NOT (R AND Clk);
S_g <= NOT (S AND Clk);
Qa <= NOT (S_g AND Qb);
Qb <= NOT (R_g AND Qa);
Q <= Qa;
END Structural;


```

Parte 3

Technology Map Viewer:

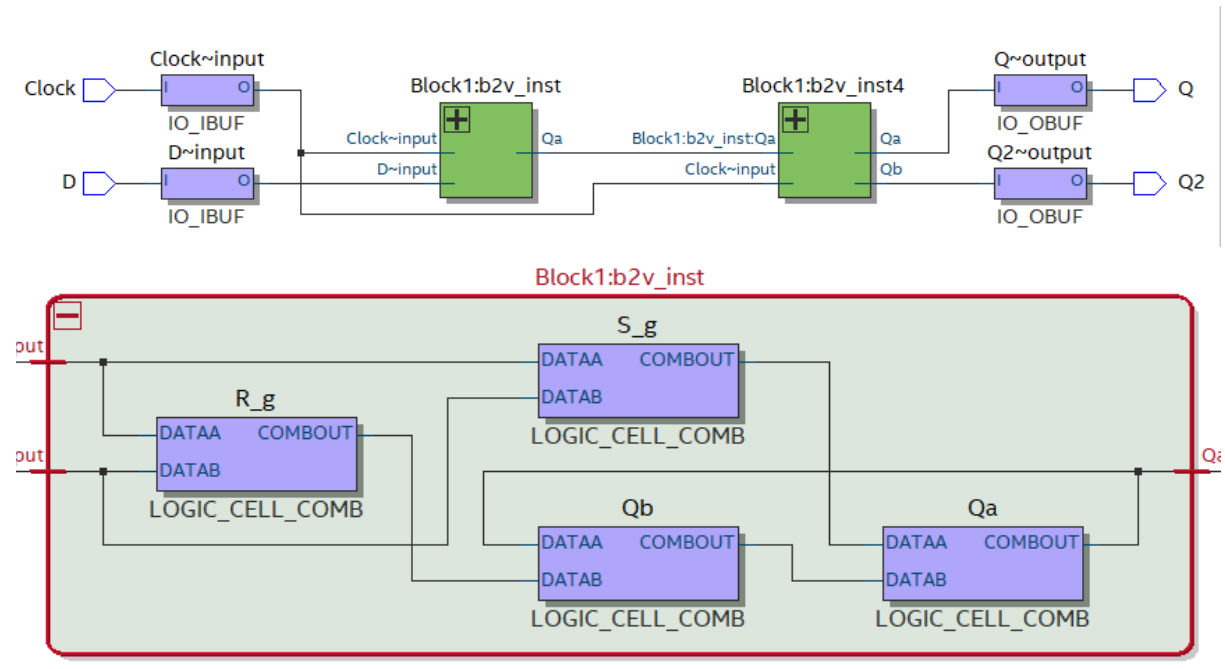

Simulação do ModelSim

 

Código VHDL:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
LIBRARY work;
ENTITY part3 IS
    PORT
    (
        D : IN STD_LOGIC;
        Clock : IN STD_LOGIC;
        Q : OUT STD_LOGIC;
        Q2 : OUT STD_LOGIC
    );
END part3;
ARCHITECTURE bdf_type OF part3 IS
    COMPONENT Block1
        PORT(D : IN STD_LOGIC;
            Clk : IN STD_LOGIC;
            Q : OUT STD_LOGIC;
            Q2 : OUT STD_LOGIC

```

```


    );
END COMPONENT;
SIGNAL      Qm : STD_LOGIC;
SIGNAL      Qs : STD_LOGIC;
SIGNAL      SYNTHESIZED_WIRE_0 : STD_LOGIC;
BEGIN
b2v_inst : Block1
PORT MAP(D => D,
          Clk => SYNTHESIZED_WIRE_0,
          Q => Qm);
SYNTHESIZED_WIRE_0 <= NOT(Clock);
b2v_inst4 : Block1
PORT MAP(D => Qm,
          Clk => Clock,
          Q => Qs,
          Q2 => Q2);


Q <= Qs;
END bdf_type;

```

Parte 4

Technology Map Viewer:

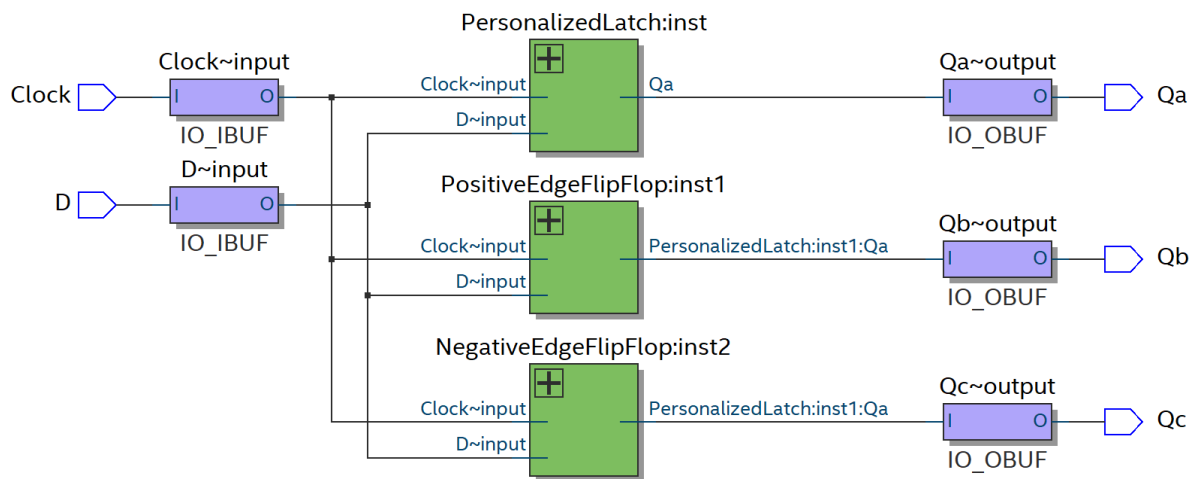

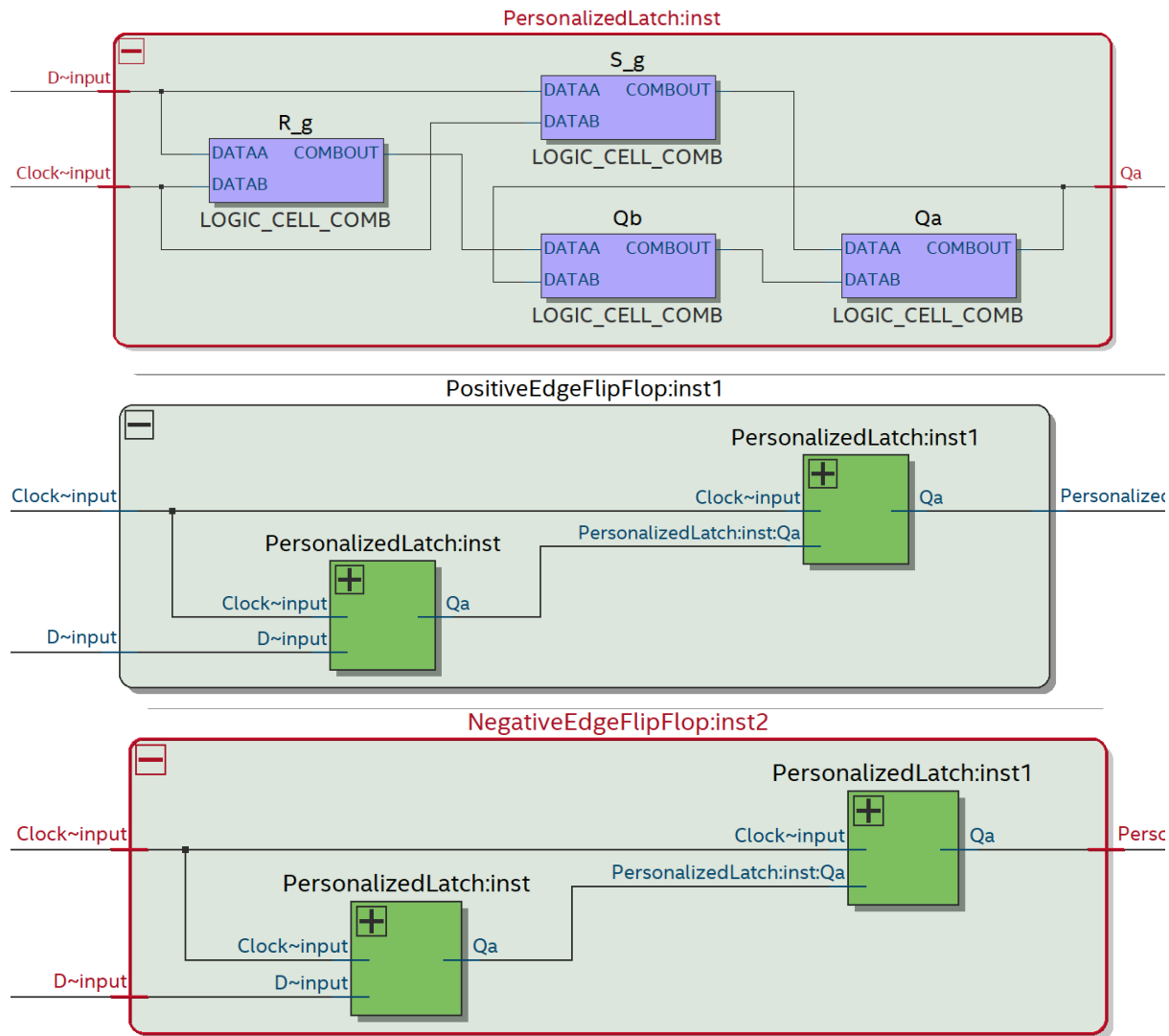

Código VHDL:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
LIBRARY work;
ENTITY part4 IS
    PORT
    (
        D : IN STD_LOGIC;
        Clock : IN STD_LOGIC;
        Qa : OUT STD_LOGIC;
        Qb : OUT STD_LOGIC;
        Qc : OUT STD_LOGIC
    );
END part4;
ARCHITECTURE bdf_type OF part4 IS

```

```

COMPONENT personalizedlatch
    PORT(D : IN STD_LOGIC;
          Clk : IN STD_LOGIC;
          Q : OUT STD_LOGIC
    );
END COMPONENT;
COMPONENT positiveedgeflipflop
    PORT(D : IN STD_LOGIC;
          Clock : IN STD_LOGIC;
          Q : OUT STD_LOGIC
    );
END COMPONENT;
COMPONENT negativeedgeflipflop
    PORT(D : IN STD_LOGIC;
          Clock : IN STD_LOGIC;
          Q : OUT STD_LOGIC
    );
END COMPONENT;
BEGIN
    b2v_inst : personalizedlatch
    PORT MAP(D => D,
             Clk => Clock,
             Q => Qa);
    b2v_inst1 : positiveedgeflipflop
    PORT MAP(D => D,
             Clock => Clock,
             Q => Qb);
    b2v_inst2 : negativeedgeflipflop
    PORT MAP(D => D,
             Clock => Clock,
             Q => Qc);
END bdf_type;

```

Código VHDL personalizedLatch:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY PersonalizedLatch IS
    PORT ( D, Clk : IN STD_LOGIC;
          Q : OUT STD_LOGIC);
END PersonalizedLatch;
ARCHITECTURE Structural OF PersonalizedLatch IS
    SIGNAL R_g, S_g, Qa, Qb, S, R : STD_LOGIC ;
    ATTRIBUTE KEEP : BOOLEAN;
    ATTRIBUTE KEEP OF R_g, S_g, Qa, Qb : SIGNAL IS TRUE;
BEGIN
    S <= D;
    R <= NOT (D);

```

```

R_g <= NOT (R AND Clk);
S_g <= NOT (S AND Clk);
Qa <= NOT (S_g AND Qb);
Qb <= NOT (R_g AND Qa);
Q <= Qa;
END Structural;

```

Código VHDL positiveEdgeFlipFlop:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
LIBRARY work;
ENTITY PositiveEdgeFlipFlop IS
    PORT
    (
        D : IN STD_LOGIC;
        Clock : IN STD_LOGIC;
        Q : OUT STD_LOGIC
    );
END PositiveEdgeFlipFlop;
ARCHITECTURE bdf_type OF PositiveEdgeFlipFlop IS
    COMPONENT personalizedlatch
        PORT(D : IN STD_LOGIC;
            Clk : IN STD_LOGIC;
            Q : OUT STD_LOGIC
        );
    END COMPONENT;
    SIGNAL SYNTHESIZED_WIRE_0 : STD_LOGIC;
    SIGNAL SYNTHESIZED_WIRE_1 : STD_LOGIC;
    BEGIN
        b2v_inst : personalizedlatch
        PORT MAP(D => D,
            Clk => SYNTHESIZED_WIRE_0,
            Q => SYNTHESIZED_WIRE_1);
        b2v_inst1 : personalizedlatch
        PORT MAP(D => SYNTHESIZED_WIRE_1,
            Clk => Clock,
            Q => Q);
        SYNTHESIZED_WIRE_0 <= NOT(Clock);
    END bdf_type;

```

Código VHDL negativeEdgeFlipFlop:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
LIBRARY work;
ENTITY NegativeEdgeFlipFlop IS
    PORT

```

```

(
    D : IN STD_LOGIC;
    Clock : IN STD_LOGIC;
    Q : OUT STD_LOGIC
);
END NegativeEdgeFlipFlop;
ARCHITECTURE bdf_type OF NegativeEdgeFlipFlop IS
    COMPONENT personalizedlatch
        PORT(D : IN STD_LOGIC;
            Clk : IN STD_LOGIC;
            Q : OUT STD_LOGIC
        );
    END COMPONENT;
    SIGNAL SYNTHESIZED_WIRE_0 : STD_LOGIC;
    SIGNAL SYNTHESIZED_WIRE_1 : STD_LOGIC;
    BEGIN
        b2v_inst : personalizedlatch
        PORT MAP(D => D,
            Clk => Clock,
            Q => SYNTHESIZED_WIRE_0);
        b2v_inst1 : personalizedlatch
        PORT MAP(D => SYNTHESIZED_WIRE_0,
            Clk => SYNTHESIZED_WIRE_1,
            Q => Q);
        SYNTHESIZED_WIRE_1 <= NOT(Clock);
    END bdf_type;

```

Simulação no ModelSim:

